



DCEL101

Reg. No.

--	--	--	--	--	--	--	--

I Semester B.Sc. Degree Examination, May/June- 2022

ELECTRONICS

Electronic Devices & Circuits

(NEP 2020 Scheme)

Paper : ELE -CT1

LIBRARY
VIJAYA COLLEGE
Jayanagar IV Block
Bangalore-560 011

Time : 2½ Hours

Maximum Marks : 60

Instructions to Candidates:

Answer all the questions from Part -A, any FOUR questions from Part-B and any FOUR questions from Part -C


Note: Answer all the questions of Part-A in any one page and to be answered only once. In this Part, answering the same question multiple times will not be considered for Evaluation.

PART -A

1. Answer All the Sub divisions

(12×1=12)

- i) The circuit whose properties are same in either direction is known as
- | | |
|-------------------------|-----------------------|
| a) Unilateral circuit | b) Bilateral circuit |
| c) Irreversible circuit | d) Reversible circuit |
- ii) For maximum transfer of power, internal resistance of the source should be
- | | |
|---------------------------------|------------------------------|
| a) equal to load resistance | b) Less than load resistance |
| c) Greater than load resistance | d) None of the above |
- iii) Theoretical value of efficiency for a full Wave Rectifier is
- | | |
|----------|----------|
| a) 40.6% | b) 81.2% |
| c) 21.0% | d) 1.21% |
- iv) Output voltage in the following circuit is
- | | |
|---------|---------|
| a) 10 V | b) 5V |
| c) -10V | d) -5 V |

 


[P.T.O.]



(2)

DCEL101

- v) The transistor gets the name BJT as the conduction is
- Due to immobile ions.
 - Due to only holes
 - Due to both holes and electrons.
 - Due to only electrons.
- vi) The correct relationship between the two current gains in BJT is
- | | |
|---------------------------------|-------------------------|
| a) $\alpha = \beta / 1 + \beta$ | b) $\alpha = 1 - \beta$ |
| c) $\alpha = \beta / 1 - \beta$ | d) $\alpha = \beta + 1$ |
- vii) The biasing circuit shown in figure is
- | | |
|---------------------------|-------------------------|
| a) Collector to base bias | b) Voltage divider bias |
| c) Emitter bias | d) Fixed bias |

 

- viii) Common collector amplifier is always used as
- | | |
|---------------------------------|--------------------|
| a) Voltage amplifier | b) Power amplifier |
| c) Impedance matching amplifier | d) audio amplifier |
- ix) What is the input voltage of an amplifier with gain of 50 to generate 10V output?
- | | |
|--------|----------|
| a) 1 V | b) 200mV |
| c) 1mV | d) 200V |
- x) Which segments of a seven segment display need to be active in order to display a decimal digit 9 ?
- | | |
|---------------------|------------------|
| a) a, c, d, e, f | b) a, b, e, f, g |
| c) a, b, c, d, f, g | d) c, d, e, f |
- xi) The BCD code for decimal number 10 is
- | | |
|--------------|--------------|
| a) 1000 0000 | b) 0101 0000 |
| c) 0000 1010 | d) 0001 0000 |



(3)

DCEL101

xii) _____ is a derived logic gate.

a) OR gate

b) XOR gate

c) NOT gate

d) AND gate

LIBRARY
VIJAYA COLLEGE
Jayanagar 1/ Block
Bangalore-560 014

PART - B

Answer any Four questions.

(4×7=28)


2. a) State Thevenin's theorem. With suitable circuit diagrams, explain the steps to Thevenise a resistive network. (5+2)
- b) Draw the input and output waveforms of HWR. (5+2)
3. a) Draw the block diagram of a regulated power supply and explain each block. (5+2)
- b) What are voltage multipliers? (5+2)
4. a) Explain the input and output characteristic curves for a transistor in CE mode. (5+2)
- b) Establish the relation between β and γ for a transistor. (5+2)
5. With a circuit diagram, explain the working of a two stage RC coupled CE amplifier and draw its frequency response. (7)
6. a) Explain with numerical example, method to convert a decimal number into Binary and Hexadecimal equivalent. (5+2)
- b) Convert binary number $111010101_{(2)}$ into Gray code equivalent. (5+2)
7. a) State and prove De Morgan's theorems. (5+2)
- b) Verify the universal property of NOR gate by realizing AND gate. (5+2)

PART - C

Answer any Four questions.

(4×5=20)

 8. Find the current through load resistor $R_L = 12 \Omega$ using Norton's theorem. (5)



9. Calculate efficiency and PIV of a FWR with an input voltage of 230V rms and load resistance of 100Ω . Given $r_d = 5 \Omega$ and turns ratio 10:1. (5)


[P.T.O.]




(4)

DCEL101

 10. Calculate I_Z (min) and I_Z (max) in the circuit shown. Given: $V_Z=10V$, $V_{in}=36V$ and $P_Z=500mW$. (5)



 11. Draw the DC load line and mark the operating point for the biasing circuit shown in figure using Silicon transistor. Given $\beta=200$. (5)



LIBRARY
VIJAYA COLLEGE
Jayanagar 17 Block
Bargalore-560 011

12. a) Subtract $20H$ from $5EH$ using 2's complement method.
b) Add $10111_{(2)}$ and $11010_{(2)}$ express the result in decimal. (3+2)
13. Simplify the Boolean expression $Y = [A\bar{B}(C + AD) + \bar{A}\bar{B}]C$ and realise using basic gates. (5)